

(in parallel) will be equal to the voltage of the power supply (in this exercise, a battery, and, thus, a DC circuit). This means that the current flow through each resistor will depend on the value of the resistance. Once again, if all the resistors have the same value, the current through each resistor will be the same ($I_1 = I_2 = I_3$). However, since current flow is like the flow of water in pipes of different diameters, the water will move through the path of least resistance. The same phenomenon occurs with current flow in circuits. Current will flow easier (more current) in the leg of the parallel circuit with the least resistance, and proportionally through the other legs based on the value of the resistors. For example, if $R_1 > R_2 > R_3$, then we have the situation where $I_1 < I_2 < I_3$. Finally, if the circuit is broken in one leg of the circuit, the current still flows through the rest of the circuit.

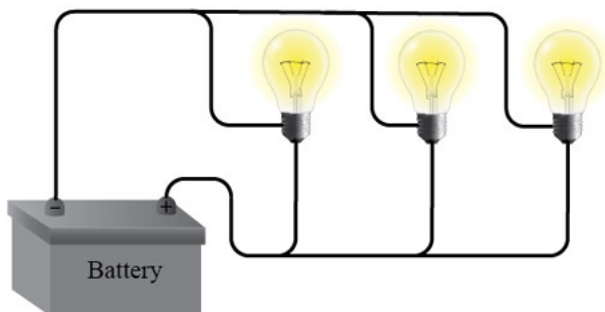


Figure 3: Parallel circuit

PROCEDURE

You will observe the experiment performed and fill in your data sheets.

- 1 Open the experiment instructions and worksheet.
 - Build an Electric Circuit Instructions (HTML or PDF)
 - Build an Electric Circuit Worksheet¹.
- 2 After you have thoroughly read the instructions and worksheet, open the experiment simulation² in which you will conduct the experiment and collect your data.
- 3 Record your data in the worksheet. Compare to the value of voltage and current predicted by Ohm's Law. (You will need it for the experiment report assignment in WebAssign.)

¹worksheet.pdf

²https://phet.colorado.edu/sims/html/circuit-construction-kit-dc-virtual-lab/latest/circuit-construction-kit-dc-virtual-lab_en.html